

Last day

If we have an inhomogeneous system with solution

$$\vec{x} = \vec{q} + \alpha_1 \vec{a}_1 + \alpha_2 \vec{a}_2 + \dots + \alpha_n \vec{a}_n$$


$\alpha_1, \alpha_2, \dots, \alpha_n$ are scalars.

If $\alpha_1 = \alpha_2 = \dots = \alpha_n = 0$, then $\vec{x} = \vec{q}$ is also a solution of the system.

Loop currents

~~eliminate~~


elementary closed loops.

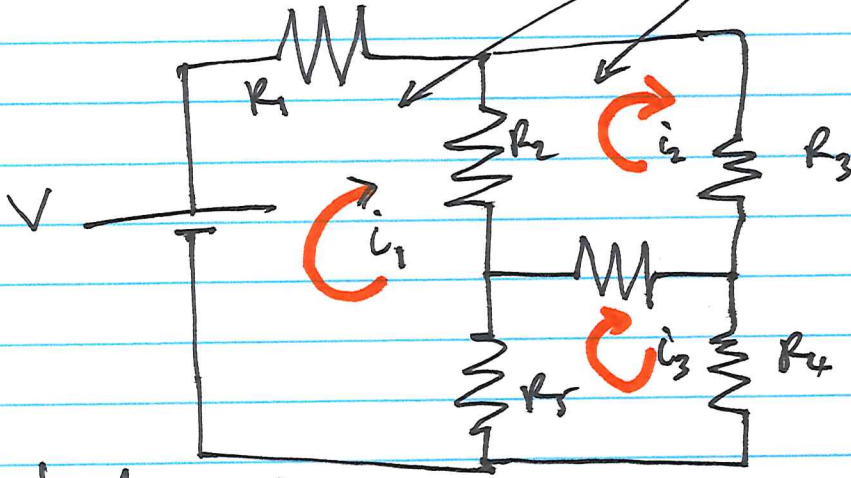

This technique:

- eliminates redundancy
- give unique solution to the system of equations.

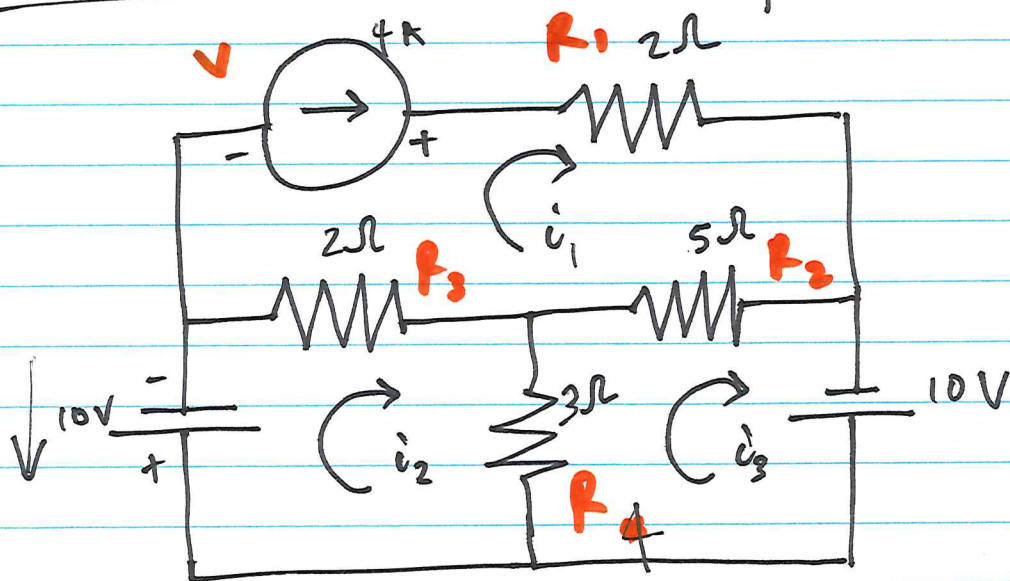Example! Solve the following ~~the~~ network



Find the current through ~~each~~ each elementary loop and the voltage through each current source.

— our unknown variables are
 V, i_1, i_2, i_3

From loop 1!

$$V = IR$$

from R_1 : $2i_1$

from R_2 : $5(i_1 - i_3)$

from R_3 : $2(i_1 - i_2)$

$$V = 2i_1 + 5(i_1 - i_3) + 2(i_1 - i_2)$$

$$9i_1 - 2i_2 - 5i_3 - V = 0 \quad \text{--- (1)}$$

From loop 2:

$$-10 = 2(i_2 - i_1) + 3(i_2 - i_3)$$

$$= 2i_2 - 2i_1 + 3i_2 - 3i_3$$

$$-10 = -2i_1 + 5i_2 - 3i_3$$

$$-2i_1 + 5i_2 - 3i_3 = -10 \quad \text{--- (2)}$$

From loop 3:

$$10 = 3(i_3 - i_2) + 5(i_3 - i_1)$$

$$-5i_1 - 3i_2 + 8i_3 = 10 \quad \text{--- (3)}$$

- look at the ^{current} ~~power~~ source.

$$i_1 = 4$$

$$9i_1 - 2i_2 - 5i_3 - V = 0$$

$$-2i_1 + 5i_2 - 3i_3 = -10$$

$$-5i_1 - 3i_2 + 8i_3 = 10$$

$$i_1 = 4$$

The augmented matrix is

$$A=0 \left(\begin{array}{cccc|c} 9 & -2 & -5 & -1 & 0 \\ -2 & 5 & -3 & 0 & -10 \\ -5 & -3 & 8 & 0 & 10 \\ 1 & 0 & 0 & 0 & 4 \end{array} \right)$$


~~By~~ using the command `ref(A)` in MATLAB, it gives

$$\left(\begin{array}{cccc|c} 1 & 0 & 0 & 0 & 4 \\ 0 & 1 & 0 & 0 & 2.3871 \\ 0 & 0 & 1 & 0 & 4.6452 \\ 0 & 0 & 0 & 1 & 8 \end{array} \right)$$

$$\Rightarrow \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ \sqrt{0} \end{pmatrix} = \begin{pmatrix} 4 \\ 2.3871 \\ 4.6452 \\ 8 \end{pmatrix}$$

from the solution of the system, we have $v=8 \rightarrow 8V$

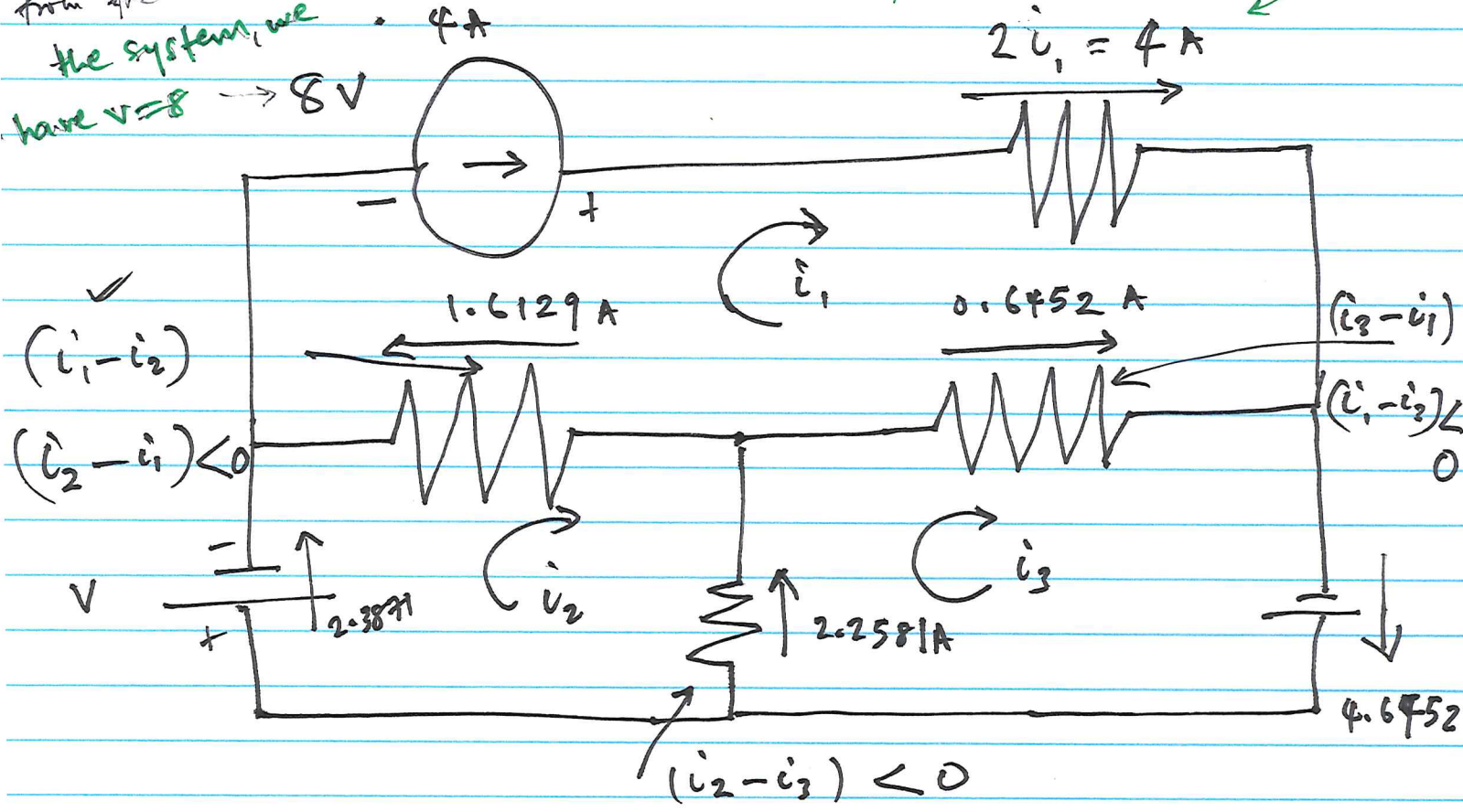$V=IR \Rightarrow i = \frac{8}{2} = 4A$
 $v=8, R=2$




$V = iR$

$I = \frac{V}{R}$

$(i_3 - i_2) \checkmark$

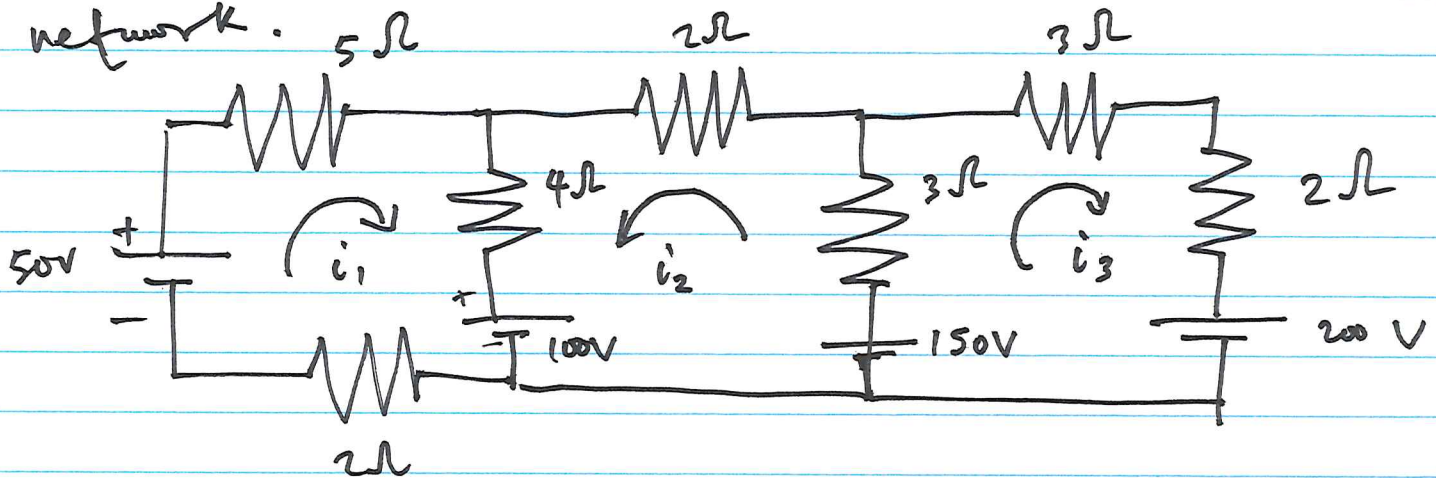Example:

Find the current in each of the branches of the network.



Our unknowns are i_1 , i_2 , and i_3

From loop 1:

$$-100 + 50 = 5i_1 + 4(i_1 + i_2) + 2i_1$$

Simplifying,

$$11i_1 + 4i_2 = -50 \quad \text{--- (1)}$$

From loop 2:

$$150 - 100 = 3(i_2 + i_3) + 2i_2 + 4(i_2 + i_1)$$

$$\Rightarrow 4i_1 + 9i_2 + 3i_3 = 50 \quad \text{--- (2)}$$

From loop 3:

$$150 - 250 = 3(i_2 + i_3) + 3i_3 + 2i_3$$

$$3i_2 + 8i_3 = -50 \quad \text{--- (3)}$$

$$11i_1 + 4i_2 = -50$$

$$4i_1 + 9i_2 + 3i_3 = 50$$

$$\cdot 3i_2 + 8i_3 = -50$$

The augmented matrix is

$$\left(\begin{array}{ccc|c} 11 & 4 & 0 & -50 \\ 4 & 9 & 3 & 50 \\ 0 & 3 & 8 & -50 \end{array} \right)$$


using rref in MATLAB, we have

$$\left(\begin{array}{ccc|c} 1 & 0 & 0 & -9.469 \\ 0 & 1 & 0 & 13.5399 \\ 0 & 0 & 1 & -11.3274 \end{array} \right)$$

$$\Rightarrow i_1 = -9.469$$

$$i_2 = 13.5399$$

$$i_3 = -11.3274$$

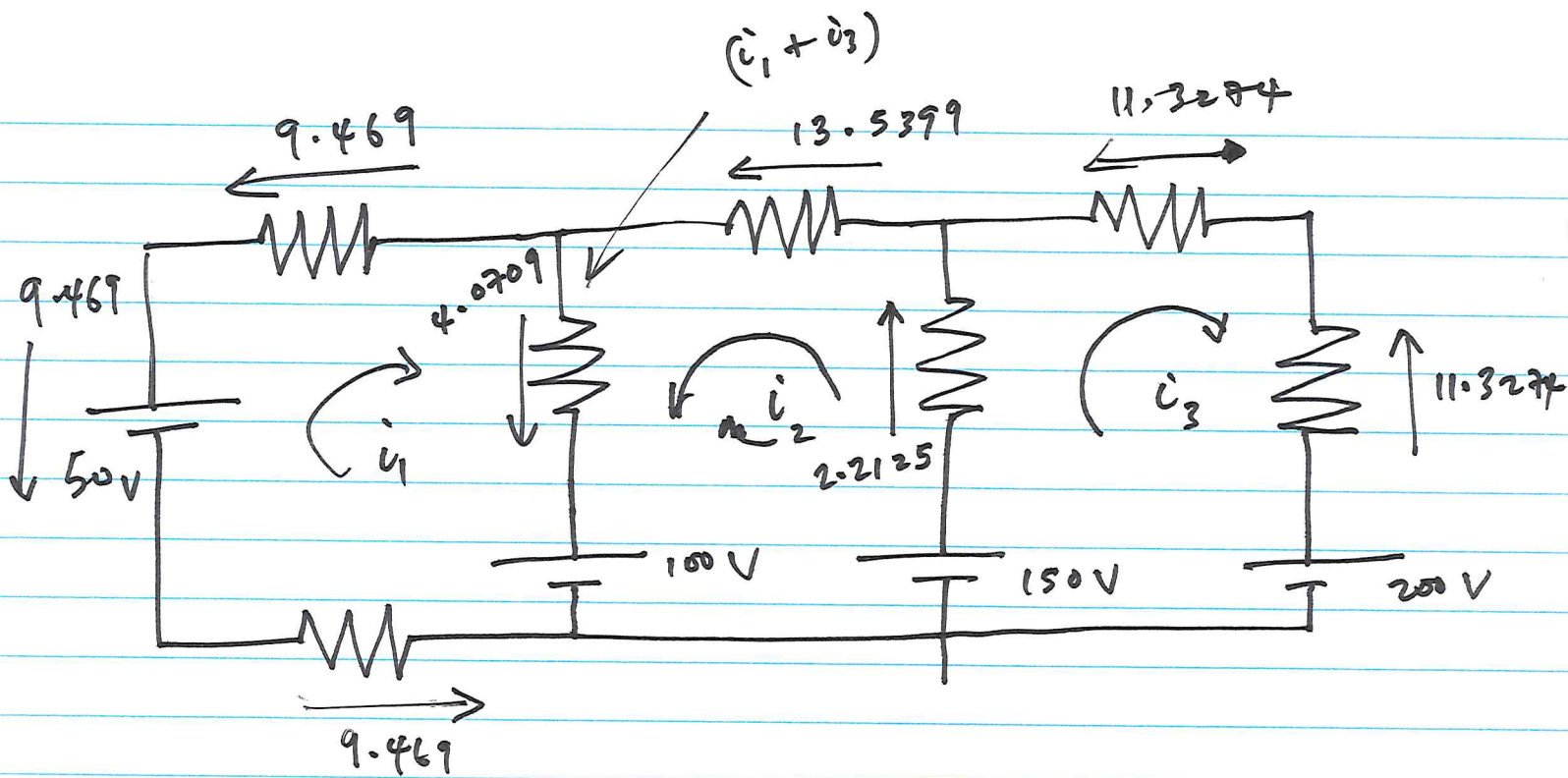

~~$V = IR$~~
 ~~$I = \frac{V}{R}$~~

~~Handwritten scribbles in red ink.~~

$a_{1,1}$

MATRIX OPERATIONS

Let A be an $n \times m$ matrix
number of rows number of columns

Eg

$$A = \begin{pmatrix} a_{11} & a_{12} & \dots & a_{1m} \\ a_{21} & a_{22} & \dots & a_{2m} \\ \vdots & \vdots & \dots & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nm} \end{pmatrix}$$

row

row

Column vector: an $1 \times n$ matrix is a column vector

vector

Eg

$$(a_1, a_2, \dots, a_n)$$

Column vector: an $m \times 1$ matrix is a column

vector

Eg

$$\begin{pmatrix} a_1 \\ a_2 \\ \vdots \\ a_m \end{pmatrix}$$

Matrix addition:

$$\text{Let } A = \begin{pmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{m1} & a_{m2} & \dots & a_{mn} \end{pmatrix}$$

$$B = \begin{pmatrix} b_{11} & b_{12} & \dots & b_{1n} \\ b_{21} & b_{22} & \dots & b_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ b_{m1} & b_{m2} & \dots & b_{mn} \end{pmatrix}$$

$$A+B = \begin{pmatrix} a_{11}+b_{11} & a_{12}+b_{12} & \dots & +a_{1n}+b_{1n} \\ a_{21}+b_{21} & a_{22}+b_{22} & \dots & +a_{2n}+b_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{m1}+b_{m1} & a_{m2}+b_{m2} & \dots & +a_{mn}+b_{mn} \end{pmatrix}$$

Scalar multiplication

Let λ be scalar and A be the same as the previous matrix.

~~Then~~ Then

$$\lambda A = \lambda \begin{pmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{m1} & a_{m2} & \dots & a_{mn} \end{pmatrix}$$

$$= \begin{pmatrix} \lambda a_{11} & \lambda a_{12} & \dots & \lambda a_{1n} \\ \lambda a_{21} & \lambda a_{22} & \dots & \lambda a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ \lambda a_{m1} & \lambda a_{m2} & \dots & \lambda a_{mn} \end{pmatrix}$$